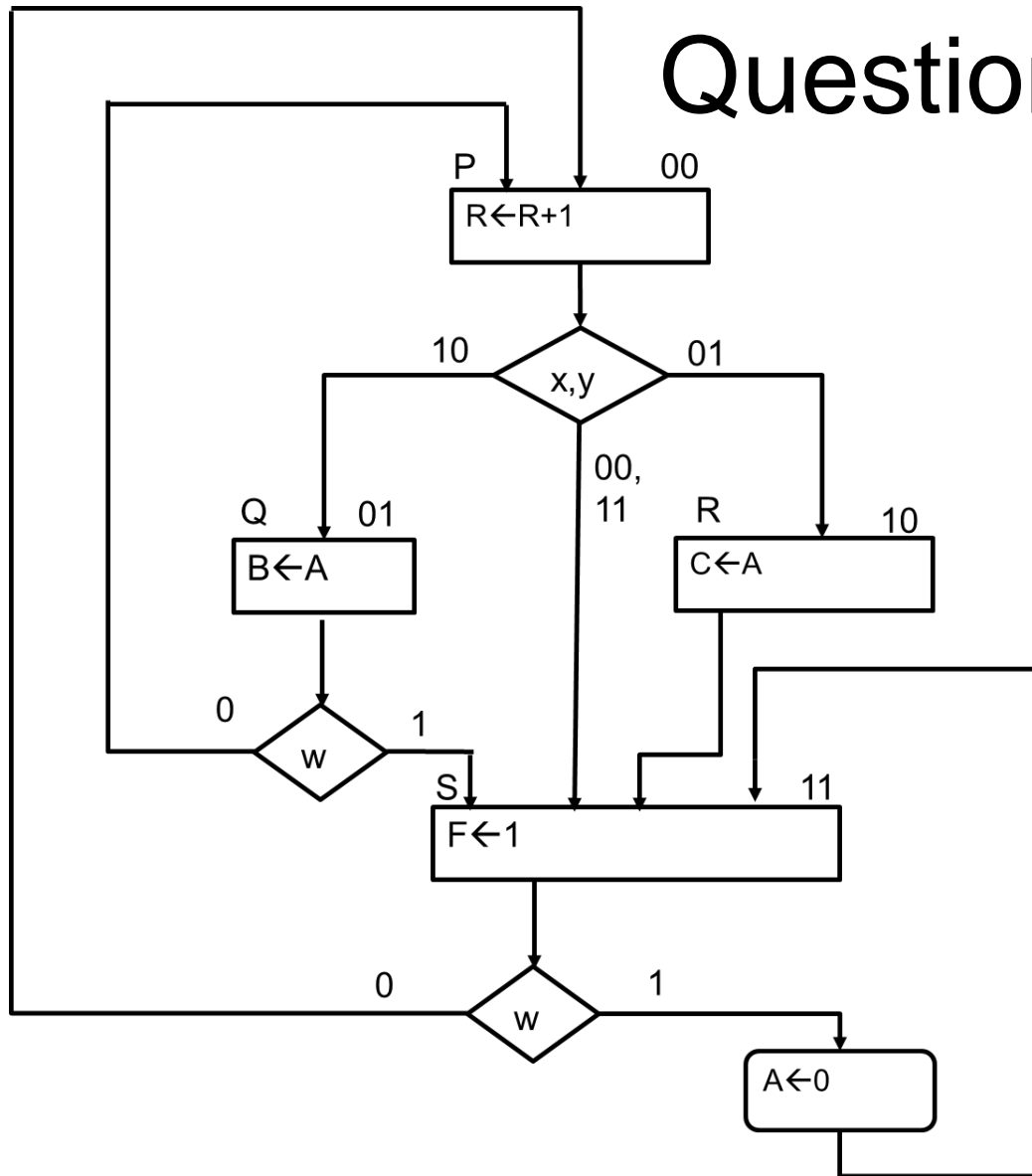


Algorithmic State Machine

Practice Questions

Question 1




Design the control unit of the given ASM chart and give its circuit diagram using all methods. Use JK FFs for the classical sequential circuit design.

Design the Datapath with a counter R, Registers A, B, C and a D-FF F.

Question 1 Solution with Multiplexer (modified D-FF)

Present State		Next State		Inputs			Outputs			
Name	G_1G_0	Name	G_1G_0	x	y	w	P	Q	R	S
P	00	S	11	0	0	-	1	0	0	0
	00	S	11	1	1	-	1	0	0	0
	00	Q	01	1	0	-	1	0	0	0
	00	R	10	0	1	-	1	0	0	0
Q	01	P	00	-	-	0	0	1	0	0
	01	S	11	-	-	1	0	1	0	0
R	10	S	11	-	-	-	0	0	1	0
S	11	S	11	-	-	1	0	0	0	1
	11	P	00	-	-	0	0	0	0	1

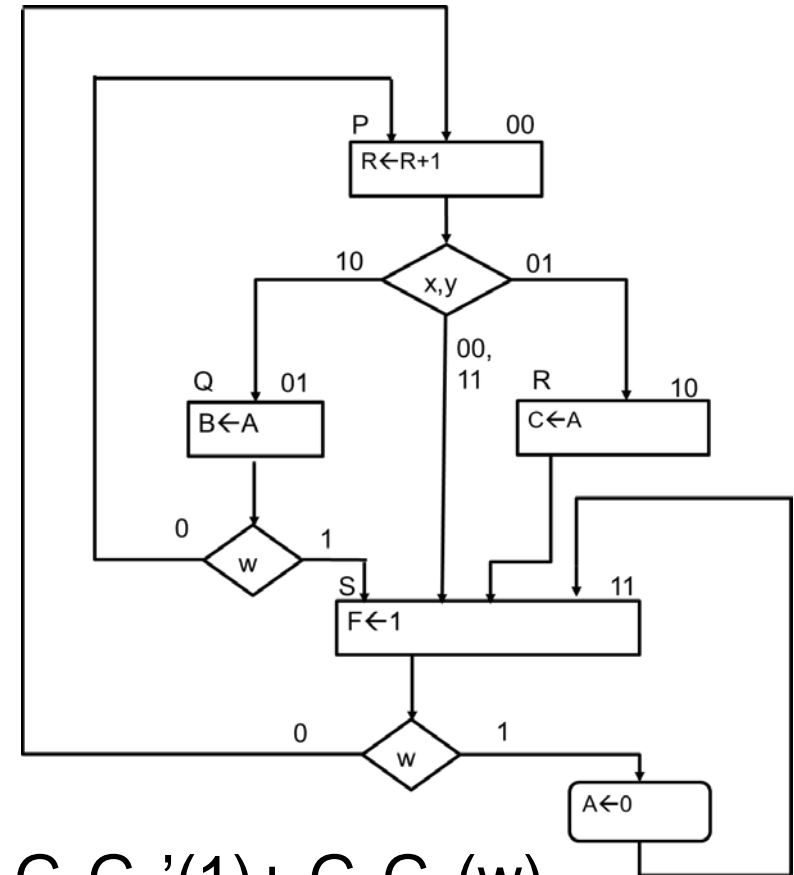


$$DG_1 = G_1'G_0'(x'y' + xy + x'y) + G_1'G_0(w) + G_1G_0'(1) + G_1G_0(w)$$

$$DG_0 = G_1'G_0'(x'y' + xy + xy') + G_1'G_0(w) + G_1G_0'(1) + G_1G_0(w)$$





Question 1 Solution

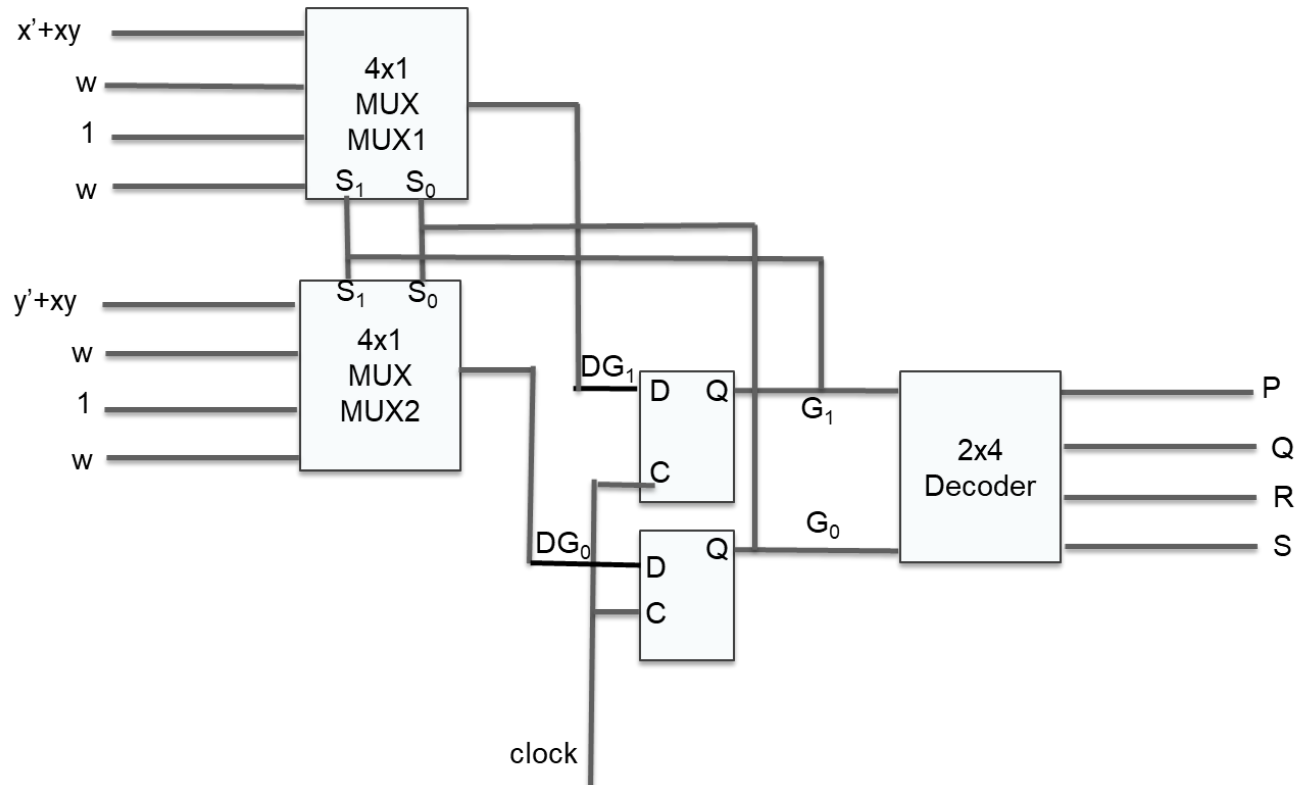

$$DG_1 = G_1'G_0'(x'y' + xy + x'y) + G_1'G_0(w) + G_1G_0'(1) + G_1G_0(w)$$

$$DG_0 = G_1'G_0'(x'y' + xy + xy') + G_1'G_0(w) + G_1G_0'(1) + G_1G_0(w)$$

Question 1 Solution

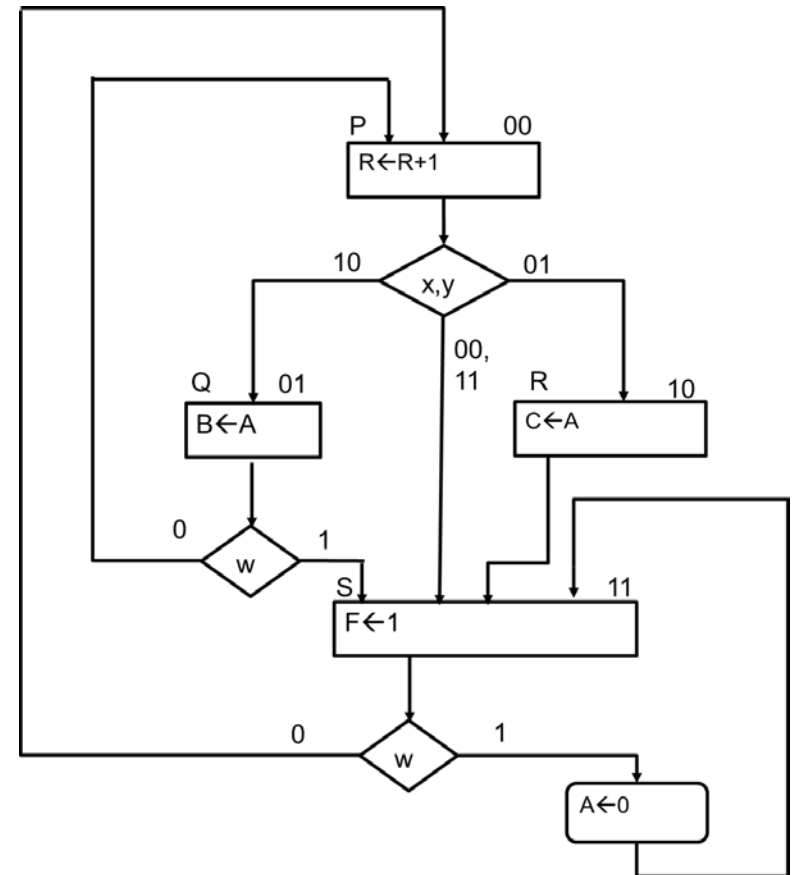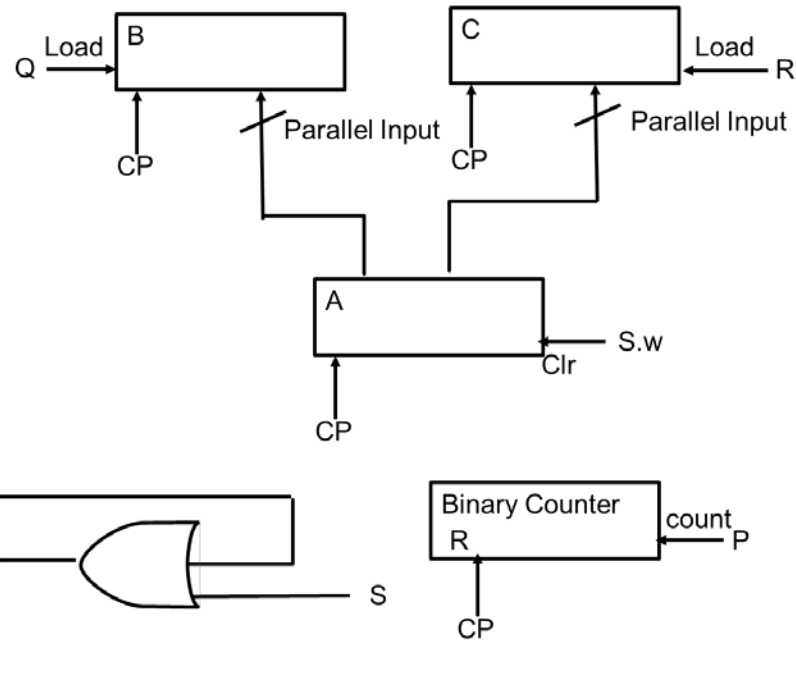

Question 2

- Registers A and B and a JK FF that is called F will function as follows:
- A start signal S initiates the operation by loading an n-bit number to register A.
- Register A has Comp_A input which loads the complement of the register value in the next clock cycle
- Then an external signal P directs the operation as follows:
- If $P=1$:
 - If the content of A is an even number, F is cleared and the content of A is transferred to register B
 - If the content of A is an odd number, F is set and the complement of the content of A is transferred to register B
- If $P=0$:
 - If the content of A is an even number, F is cleared and the complement of the content of A is transferred to register B
 - If the content of A is an odd number, F is set and the content of A is transferred to register B



Question 2


- Draw an ASM chart using a minimum number of state boxes.
- Draw the Data path circuit diagram
- Design the control unit using all methods. Use JK FFs for the classical sequential circuit design.



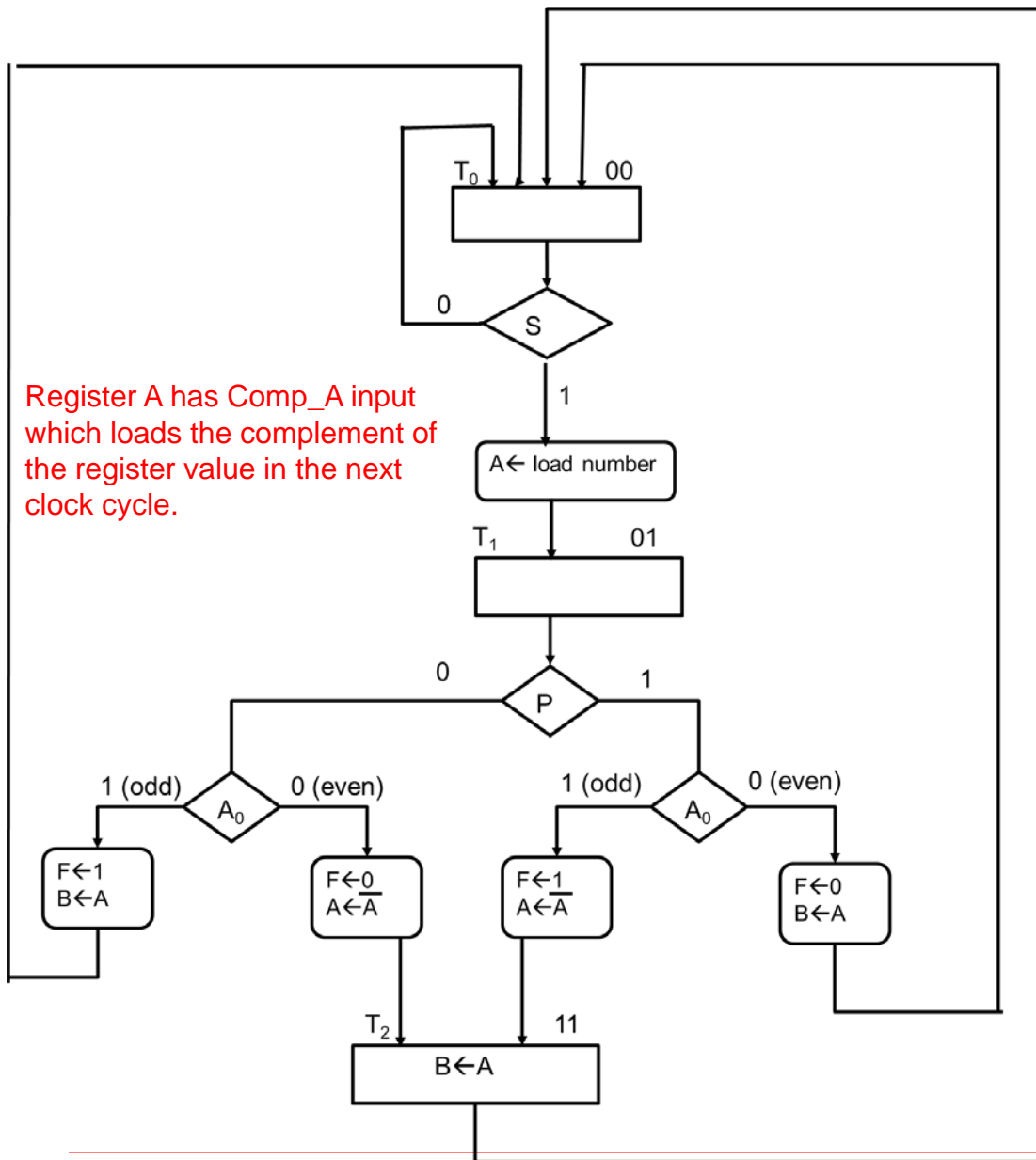Question 2 Solution


- A start signal S initiates the operation by loading an n-bit number to register A.
- **Then**
- If $P=1$:
 - If the content of A is an even number, F is cleared and the content of A is transferred to register B
 - If the content of A is an odd number, F is set and the complement of the content of A is transferred to register B
- If $P=0$:
 - If the content of A is an even number, F is cleared and the complement of the content of A is transferred to register B
 - If the content of A is an odd number, F is set and the content of A is transferred to register B

Register A has Comp_A input which loads the complement of the register value in the next clock cycle.



Question 2 Solution

Present State		Next State		Inputs			Outputs		
Name	G_1G_0	Name	G_1G_0	S	P	A_0	T0	T1	T2
T0	00	T_0	00	0	-	-	1	0	0
	00	T_1	01	1	-	-	1	0	0
T1	01	T_0	00	-	1	0	0	1	0
	01	T_0	00	-	0	1	0	1	0
	01	T_2	11	-	1	1	0	1	0
	01	T_2	11	-	0	0	0	1	0
T2	11	T_0	00	-	-	-	0	0	1

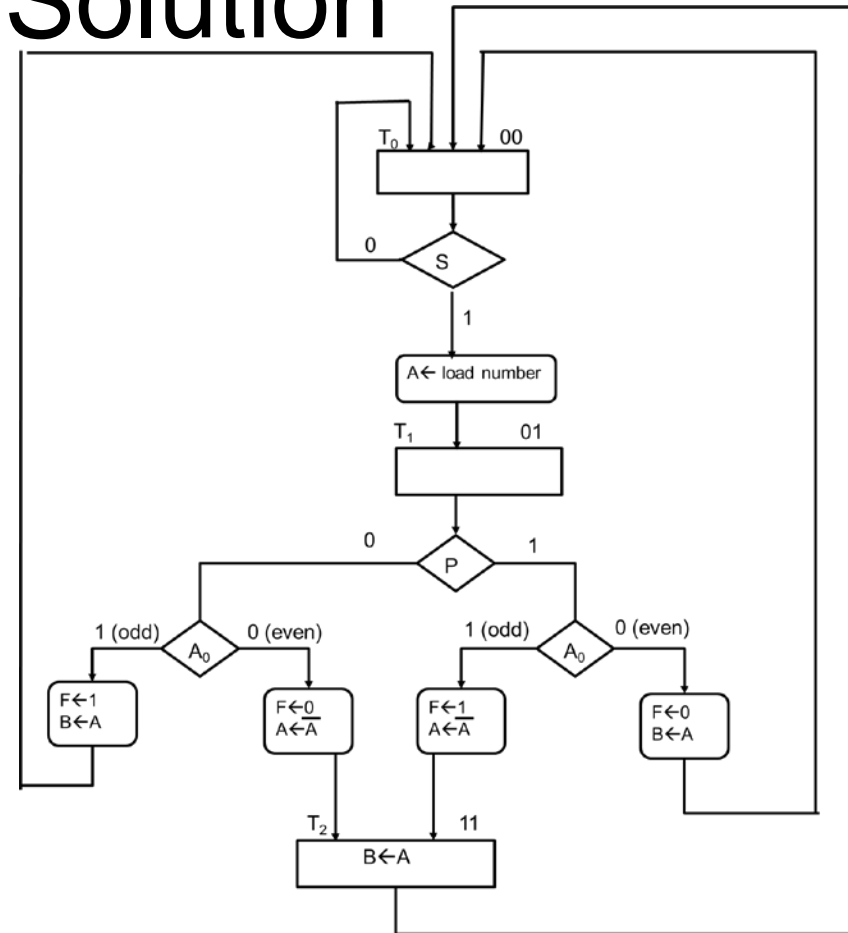


$$DG_0 = G_1'G_0'S + G_1'G_0PA_0 + G_1'G_0P'A_0'$$

$$DG_1 = G_1'G_0PA_0 + G_1'G_0P'A_0'$$



Question 2 Solution

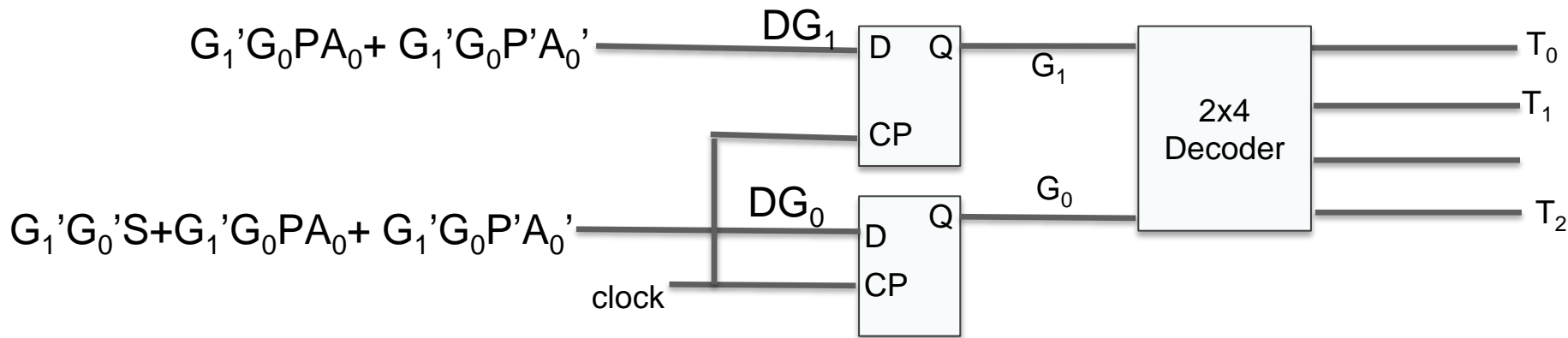

$$DG_0 = G_1'G_0'S + G_1'G_0PA_0 + G_1'G_0P'A_0'$$

$$DG_1 = G_1'G_0PA_0 + G_1'G_0P'A_0'$$



Question 2

Solution

Load_A: $S.T_0$


Comp_A: $P.A_0.T_1 + P'.A_0'.T_1$

Load_B: $P'A_0T_1 + PA_0'T_1 + T_2$


Clr_F: $A_0'T_1$

Set_F: A_0T_1

$$J = A_0T_1Q_t', K = A_0'.T_1.Q_t$$

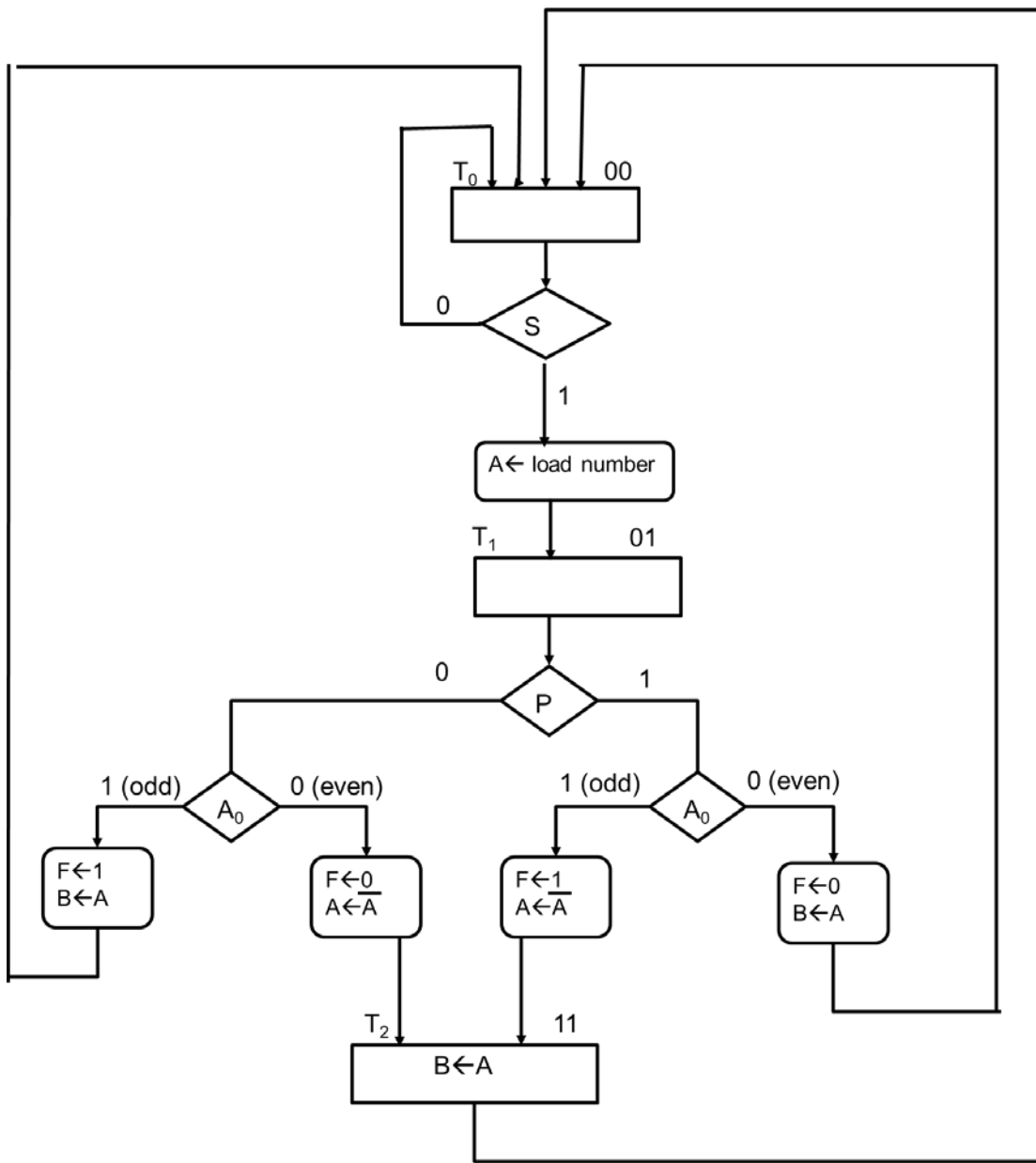

Question 2 Solution

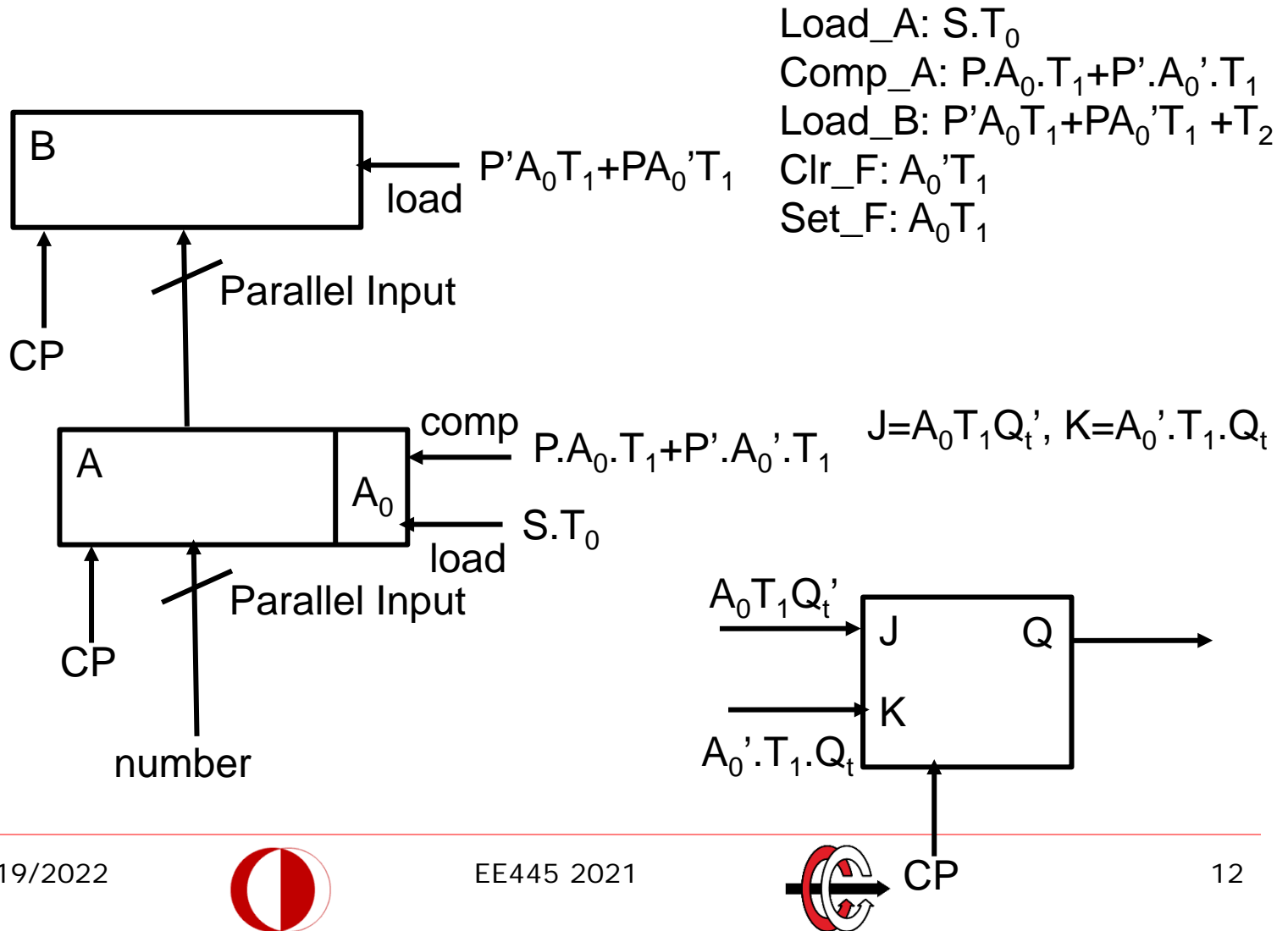

Question 3

- Design and draw the typical cell A_i of register A as specified below using formal design method with a JK FF.
 - P1: $A \leftarrow B$
 - P2: $A \leftarrow A.B$
- The combinational circuit should be minimum.
- Show all steps of the design.
- Assume that $P1.P2=0$ is always satisfied.



Question 3

Solution



$P_2 P_1$	$A\bar{B}$	$\bar{A}B$	$\bar{A}\bar{B}$	$JA\bar{B}$	$KA\bar{B}$
0 0	X	X		0	0
0 1	0	0		0	X
0 1	0	1		0	X
0 1	1	0		X	1
0 1	1	1		X	0
1 0	0	0		0	X
1 0	0	1		1	X
1 0	1	0		0	X
1 0	1	1		1	0
1 1	X	X		X	X


$$JA\bar{B} = B\bar{C} P_1$$

$$KA\bar{B} = B\bar{C}' P_2 + B\bar{C} P_1$$

Excitation

$Q\bar{Q}$	J	K
0 0	0	X
0 1	1	X
1 0	X	1
1 1	X	0

  

 

Algorithmic State Machine

Practice Questions
